

[56. 送1]

$$e_{gA} = e_{gB} = e_g = \frac{I_0 Z}{2}$$

鉄塔Aの電位上昇 e_{gA} と e_{gB}

$$e_{gA} + e_{gr} = e_{gx} = i_{gr} R \quad \text{--- ①}$$

$$i_{gA} - i_{gr} = i_{gx} + i_r \quad \text{--- ②}$$

$$i_{gA} = \frac{e_{gA}}{Z}$$

$$i_{gr} = \frac{e_{gr}}{Z}$$

$$i_{gx} = \frac{e_{gx}}{Z}$$

②より

$$\frac{e_{gA}}{Z} - \frac{e_{gr}}{Z} = \frac{e_{gx}}{Z} + \frac{e_{gx}}{R}$$


$$R(e_{gA} - e_{gr}) = (R+Z)e_{gx} \quad \text{--- ③}$$

①より









$$2e_{gA} = \frac{R+Z}{R} e_{gx} + e_{gx}$$

$$e_{gA} = \frac{2R+Z}{2R} e_{gx} \quad \therefore e_{gx} = \frac{2R}{2R+Z} e_{gA} = \frac{2R}{2R+Z} \cdot \frac{I_0}{2} Z = \frac{RZ}{2R+Z} I_0 //$$

雷撃電流 I_0

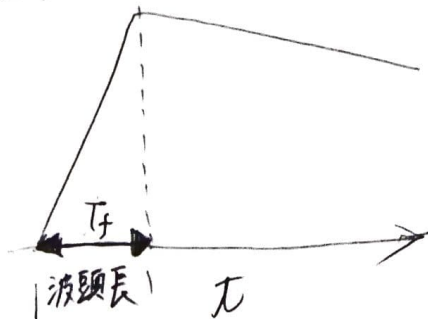

鉄塔電位の1/2 $\frac{d}{c} > T_f$

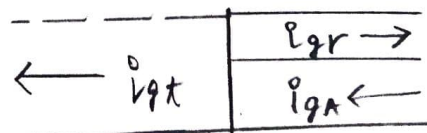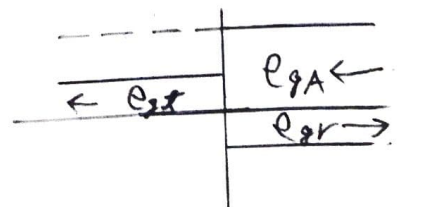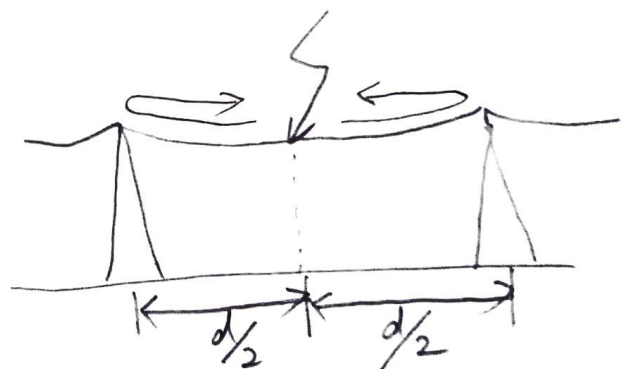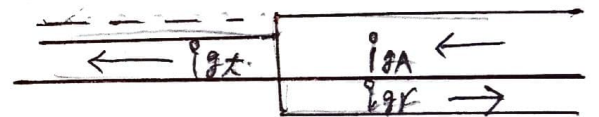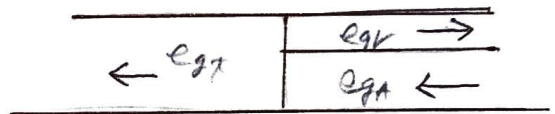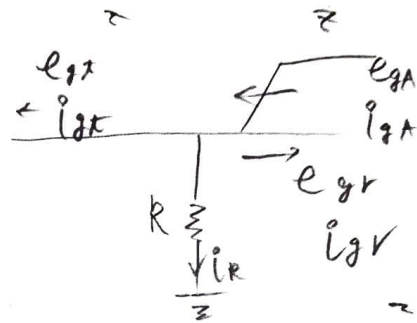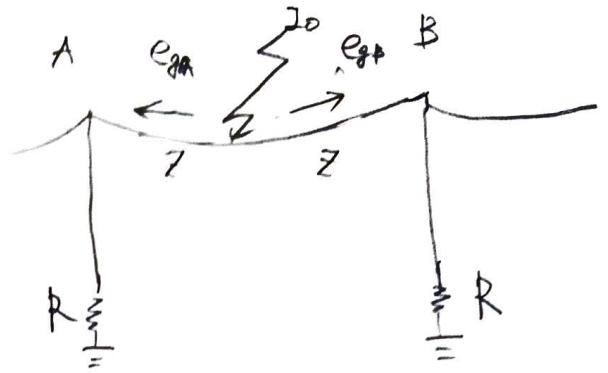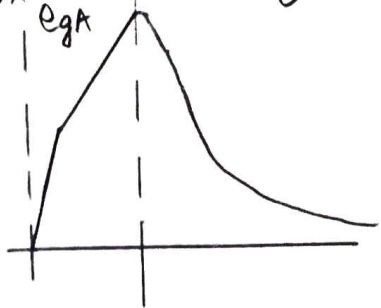

反射係数が負の場合 (負反射と呼ぶ)